
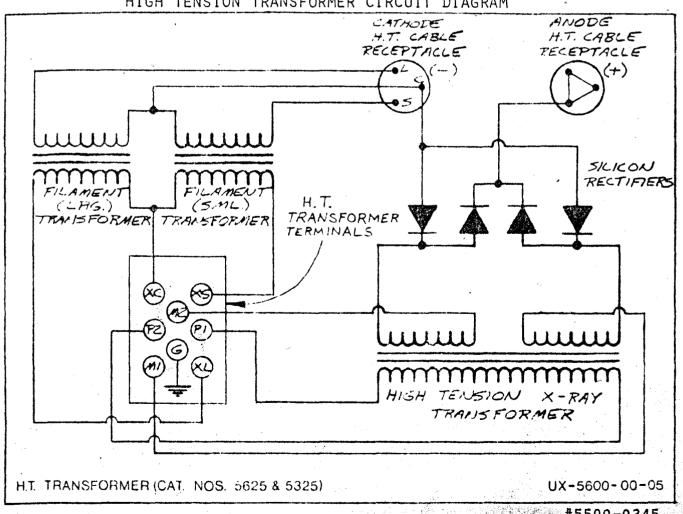


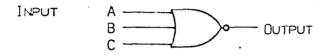HIGH TENSION TRANSFORMER CIRCU'IT DIAGRAM




SOLID STATE LINEAR X-RAY CONTACTOR/TIMER MODULE:
THE LOGIC AND CONTROL CIRCUITRY FOR THIS MODULE WAS DESIGNED WITH NPN POSITIVE DISCREET LOGIC. THE TRUTH TABLE FOR A NOR GATE IS AS SUCH:

INPUTS.			DUTPUT	
Α	В	C		
0	0	0	1	(HIGH)
1	0	0	. 0	(LOW)
0	1	0 % (4.6)	0	
1	1	0	0	
0	0	1	0	
1	0	1 .	0	
0	1	1	0	
1	1	1	0	,




THE SEQUENCING OF EVENTS OCCURES WITH AN EXPOSURE CONTACT CLOSURE AT PIN 24 OF THE SCR TIMER P.C.B. THIS OCCURS WHEN RELAY K_{2G} : IS ACTIVATED. A NO (NORMALLY OPEN) CONTACT FROM THIS RELAY IS USED TO START THIS SEQUENCING AND ALSO THE TWO BACK-UP CONTACTORS ARE PULLED IN AT THIS TIME.

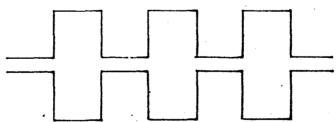Two complementary signals are generated that are synchronous to the line voltage phase, these signals at the collectors of Q3 and Q4 are:



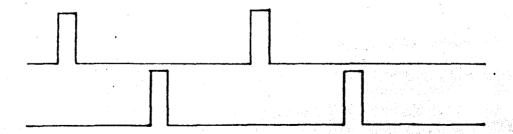
THESE SIGNALS ARE DIFFERENTIATED (${\rm C_1}$ AND ${\rm C_2}$) AND AMPLIFIED AND ARE DESIGNATED L (LINE) AND T (LINE NOT), AND OCCUR EACH 16.7 MILLISECONDS.



ALL DIGITAL SIGNAL PROCESSING IS DONE WITH L AND L. NOR GATES 9 AND 10 ACT AS A FLIP-FLOP AND ARE CONDITIONED BY L AND L WHEN THE INHIBIT BUS (CR. AND CR.) IS LIFTED. THE TWO OUTPUTS OF THIS FLIP-FLOP ARE THE DRIVING SIGNALS FOR TRANSISTORS Q. AND Q. WHICH DRIVE THE PRIMARY WINDING OF THE PULSE TRANSFORMER TR-2. THE TWO SECONDARY WINDINGS OF TR-2 DRIVE THE GATES OF SCR'S THAT ARE IN SERIES WHITH THE HIGH-TENSION TRANSFORMER. WHEN THESE SCR'S ARE TURNED ON, THE X-RAY OUTPUT IS ACHIEVED THROUGH THIS HIGH-TENSION TRANSFORMER.

WHEN THE MERCURY WETTED RELAY $K_{\rm c}$ is activated, a contact closure $K_{\rm c}$ applies an integrated signal to transistor $Q_{\rm c}$ turns on, and when $Q_{\rm l}$ 6 is conditioned, then nor gate 17 is turned off. This gives a start of count to the linear timer, since the two inhibits clamping the timer are now lifted (CR_ and CR_). The capacitor $C_{\rm c}$ now charges up in a linear slope due to the constant current source established by $Q_{\rm g}$ and the programmed external timing resistor.

8 VOLTS

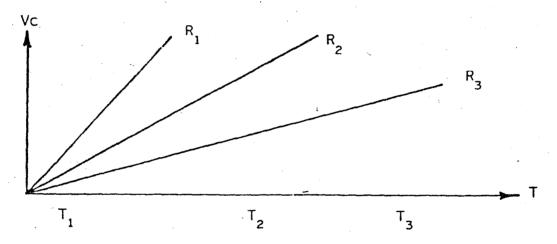

THIS TIMING CAPACITOR WILL CHARGE UP TOWARD THE +15 VOLT SUPPLY ESTABLISHED BY THE ZENER ACTION OF CR. THE FET SOURCE FOLLOWER ACTS AS AN UNLOADED OUTPUT AND TRANSISTORS Q AND Q ACT AS A TRIGGER THAT IN TURN GATES NOT 12 TO FORM AN END OF COUNT. THE TRIGGER IS SET AT APPROXIMATLEY 8 VOLTS OF CHARGE ON THE TIMING CAPACITOR.

AT THE END OF COUNT, THE GATE PULSES TO THE SCR'S IS DISCONTINUED AND THE EXPOSURE TIME IS ENDED.


NOR GATES 17 AND 18 ACT AS A FLIP-FLOP, AND THE START OF COUNT SIGNAL (NOR 17 GGES HIGH) IS ACHIEVED WHEN Q, TURNS ON AND Q IS CONTINUED. THIS HAPPENS WHEN A DIFFERENTIATED PULSE FROM EITHER C, OR C, IS "OR" GATED THROUGH CR, OR CR, AND TURNS ON Q, . THE DIFFERENTIATED PULSE IS ACHIEVED WHEN THE FLIP-FLOP FORMED BY NOR 9 AND NOR 10 IS TOGGLED. THIS FORMS THE BASIS FOR THE "CORE MEMORY" OF THE UNIT.

NOR GATES 7 AND 8 ARE SLAVED TO THE LINE AND LINE NOT SIGNALS. THEY ALSO FORM A FLIP-FLOP. THEIR OUTPUTS ARE USED TO CONDITION NOR GATES 9 AND 10 TOGETHER WITH THE OUTPUTS OF NOR 9 AND 10 OF THE CONTACTOR P.C.B., AND THE OUTPUT OF \mathbf{Q}_1 .

THE CORE MEMORY IS ACHIEVED DUE TO THE RELATIONSHIP OF THE DUTPUTS OF NOR 9 AND NOR 10 TO THE DRIVING TRANSISTORS Q, AND Q, WHICH EITHER SET OR RESET THE CORE OF THE TR2 PULSE TRANSFORMER. A SET (Q, ON) WILL FIRE ONE OF THE TWO SCR'S, AND A RESET (Q ON) WILL FIRE THE ALTERNATE SCR. THE ASSOCIATED SCR CONDUCTION IN RELATION TO THE LINE VOLTAGE IS THE BASIS FOR THE "CORE MEMORY".

TIMING RESISTORS

SWITCH POSITION	# OF PULSES	TIME (SEC.)	SELECTABLE RESISTOR (All 1% Resistors)
1	1	1/120	392
2	2	1/60	845
3	3	1/40	1.24K
4	4	1/30	1.87K
5	5	1/24	2.32K
6	6	1/20	2.74K
7	8	1/15	4.02K
. 8	10	1/12	4.99K
9	12	1/10	5.9K
10	18	3/20	9.09K
11	24	1/5	12K
12	30	1/4	15K
13	36	3/10	18K
14	48	2/5	23.7K
15	60	1/2	30.1K
16	90	3/4	45.3K
17	120	1	60.4K
18	150	1-1/4	75K
19	180	1-1/2	90.9K
20	240	2	121K
21	300	2-1/2	150K
22	360	3 ,	178K
23	720	6	365K

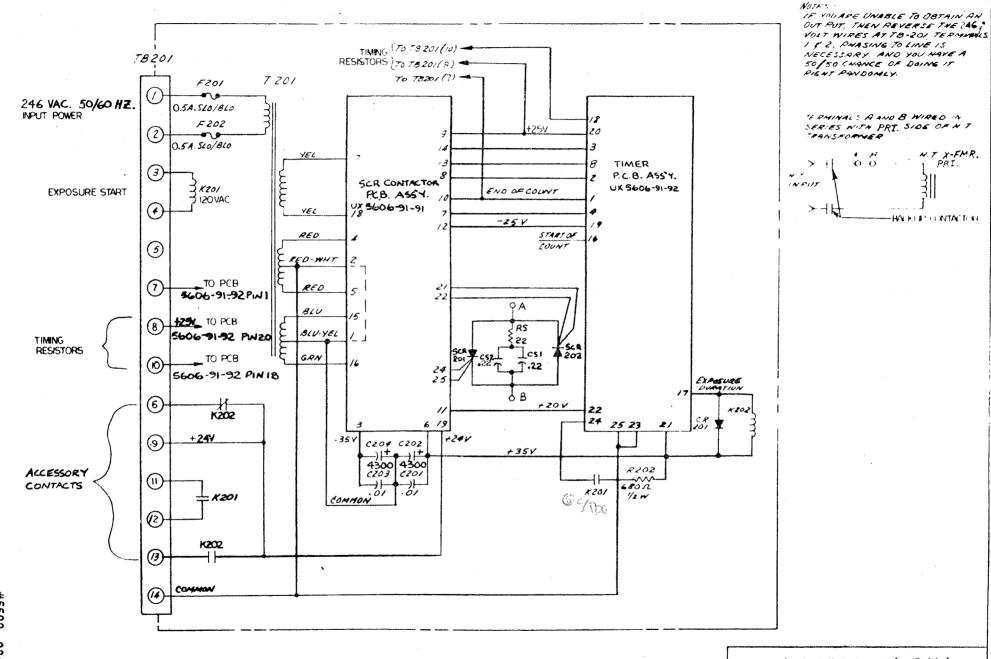



#5500-0344/0345 page 35


UNIVERSAL X-RAY

OVERALL WIRING DIAGRAM

SERGE 91-00:

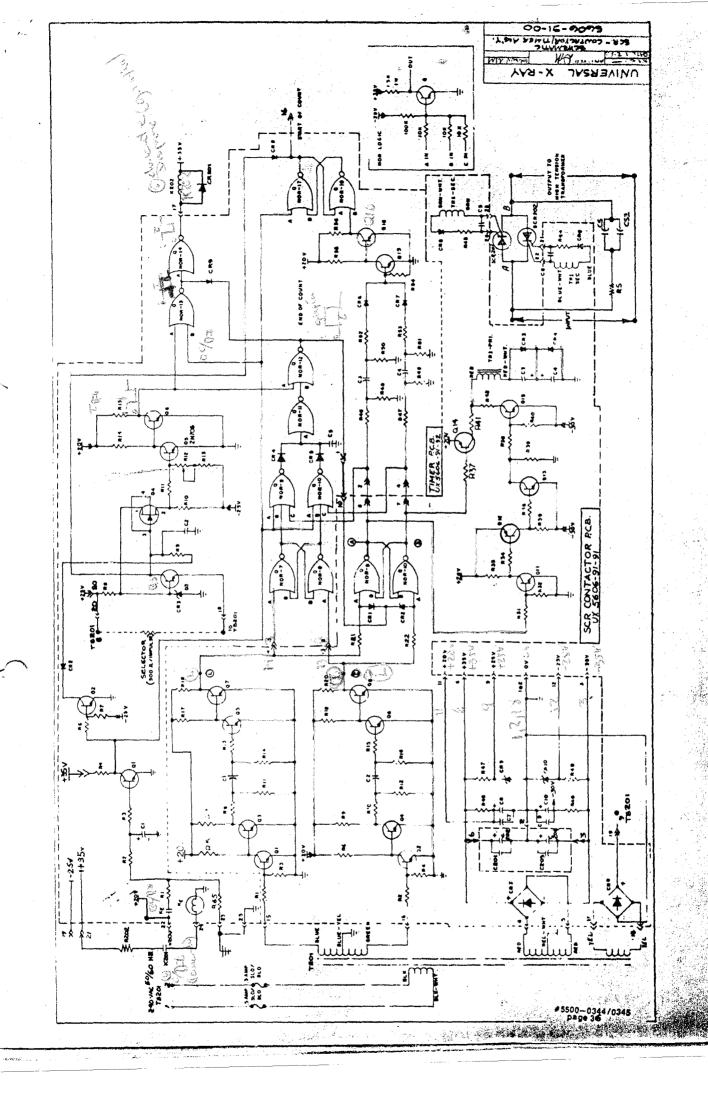

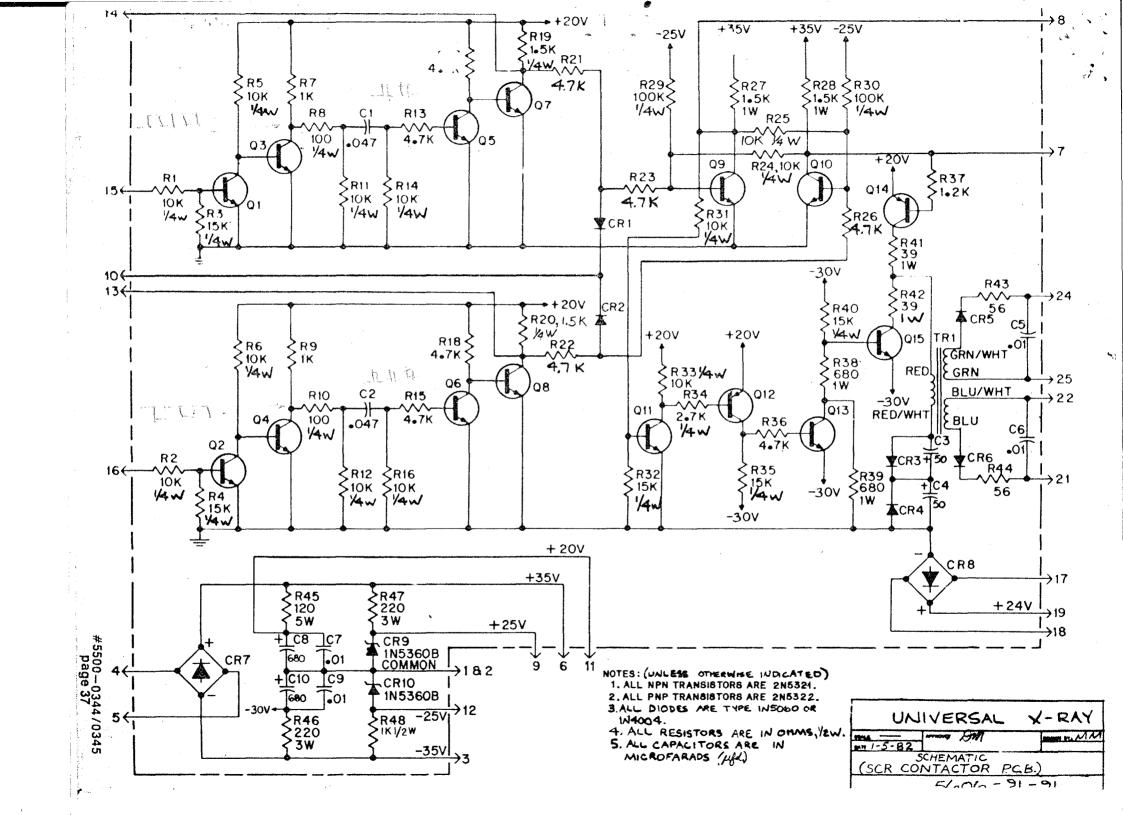

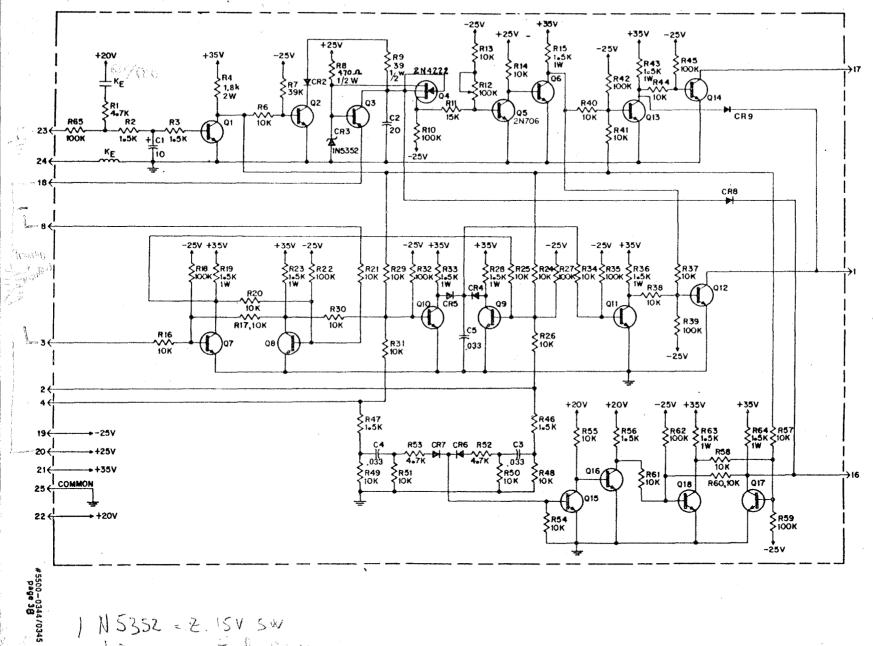

NOTE: UNIESS OTHERWISE INDICATED

- HALL NPN TRANSISTORS ARE
- 2) ALL PNP TRANSISTORS ARE TYPE 2N5322.
- 3) ALL DIODES ARE TYPE
- 4) ALL RESISTORS ARE IN OHMS 74W.
- 5) AL . CAPACITORS' ARE IN MICROFARADS.

1 N5352 = 2.15V SW se dans y no corta de dioporo

UNIVERSAL X-RAY MACK APPROJER SCHEMATIC (TIMER PLB.) 5606-91-92